


## SISTEMI TRIFASE

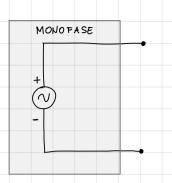

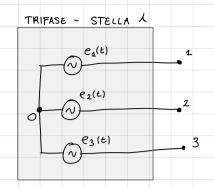

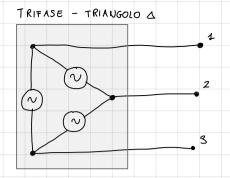


Faceudo riferimento alla conf a L


endo riferimento alla confa 
$$+\frac{2}{3}$$
 +  $\frac{2}{3}$  =  $\frac{4}{3}$  =


$$e_{1}(t) = U_{1}$$
  
 $e_{2}(t) = U_{2}$   
 $e_{3}(t) = U_{3}$ 

## TERNA SIMMETRICA

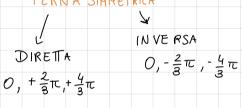
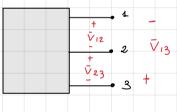
$$\bar{E}_{1} = E_{0} \qquad 2\pi U \qquad 2\pi U \qquad 2\pi U \qquad E_{2} = E_{0} \qquad E_{3} = E_{0} \qquad E_{0} = E_{0} \qquad E_{$$




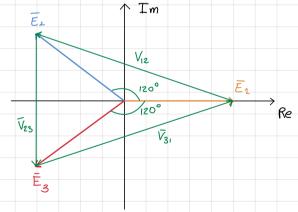
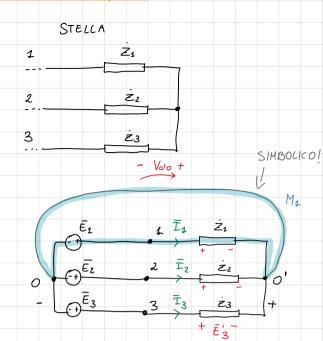
## V12 + V23 + V31 = 0

dim: LKTH: V12+ V23+ V13 = 0 oppure con le regole dei rettori





Se 
$$\overline{E}_{4} \neq \overline{E}_{2} \neq \overline{E}_{3}$$
 e  $\overline{Z}_{4} \neq \overline{Z}_{2} \neq \overline{Z}_{3}$   
=P  $\overline{V}_{12} \neq \overline{V}_{23} \neq \overline{V}_{31}$ ,  $\overline{T}_{4} \neq \overline{T}_{2} \neq \overline{T}_{3}$ 

(1) 
$$LKC_0$$
:  $\overline{I}_4 + \overline{I}_2 + \overline{I}_3 = 0$ 


(2) Vedo Vojo come la d.d.p. tra i due centri Stella


-D LKT : 
$$\overline{E}_{1}$$
 -  $\overline{E}_{1}$  +  $\overline{V}_{00}$  = 0 -0  $\int \overline{E}_{1}' = \overline{E}_{1}$  -  $\overline{V}_{00}$   $\int \overline{E}_{2}' = \overline{E}_{2}$  -  $\overline{V}_{00}$   $\int \overline{E}_{3}' = \overline{E}_{3}$  -  $\overline{V}_{00}$   $\int \overline{E}_{00}' = \overline{E}_{3}' = \overline{E}_{3}$  -  $\overline{V}_{00}$   $\int \overline{E}_{00}' = \overline{E}_{00}' =$ 


(3) Siccome 
$$\bar{T} = \frac{\bar{E}}{z}$$

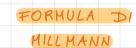(4) Trovo Vo'o

$$-0 \quad \overline{V_{0'0}} = \frac{\dot{y_2} E_1 + \dot{y_2} E_2 + \dot{y_3} E_3}{\dot{y_4} + \dot{y_2} + \dot{y_3}}$$



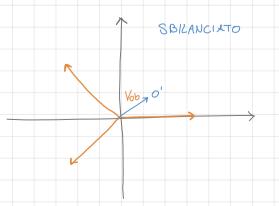

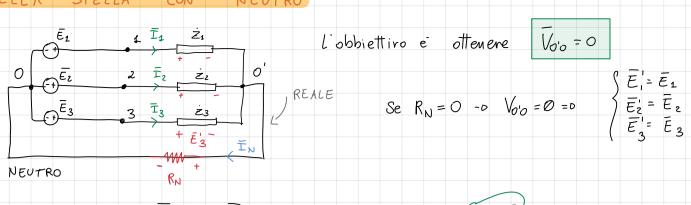





$$\begin{cases} \overline{E}_{1}^{1} = \overline{E}_{1} \\ \overline{E}_{2}^{1} = \overline{E}_{2} \\ \overline{E}_{3}^{1} = \overline{E}_{3} \end{cases}$$

ma se 
$$R_N \neq 0$$
  $\rightarrow \overline{V}_{00} = R_N \cdot \overline{I}_N \neq \emptyset$   $= \circ$   $P_N = |\overline{V}_N| \cdot |\overline{I}_N| = |\overline{R}_N \cdot |\overline{I}_N| \neq 0$ 

$$= \circ \quad P_{N} = |\overline{V}_{N}| \cdot |\overline{T}_{N}| = \left(R_{N} \cdot |\overline{T}_{N}|\right) \neq 0$$

## NO MESSA A TERRA

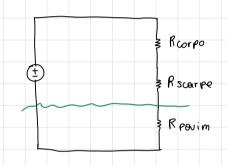

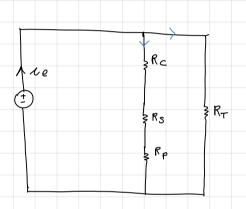

Se RT << RC+ RS+ RP

```
POTENZA
                   Abbiamo una T.S.D. con Carico Bilanciato - \overline{E}_1' = \overline{E}_1, \overline{E}_2' = \overline{E}_2, \overline{E}_3' = \overline{E}_3
         HP.
                               LD E1 + E2 + E3 =0
                                                                                     \begin{cases} 21(t) = \sqrt{2} \text{ To } \cos(\omega t - \varphi) \\ 22(t) = \sqrt{2} \text{ To } \cos(\omega t - \frac{2}{3}\pi - \varphi) \\ 23(t) = \sqrt{2} \text{ To } \cos(\omega t - \frac{4}{3}\pi - \varphi) \end{cases}
         (e1(t) = VZ to Cos(wt)
         \begin{cases} e_2(t) = \sqrt{2} & \text{Eo } Cos(\omega t - \frac{2}{3}\pi) \\ e_3(t) = \sqrt{2} & \text{Eo } Cos(\omega t - \frac{4}{3}\pi) \end{cases}
= P (t) = P1(t) + P2(t) + P3(t) = 2 E0 I0 (Wt) (ws (wt-4)+
                                                                                          + Cos(wt-2π)· Cos(wt-2π-4) +
                                                                                          + \cos(\omega t - \frac{4}{3}\pi) \cdot \cos(\omega t - \frac{4}{3}\pi - \varphi)
                      2\cos(x)\cos(y) = +\cos(x+y)\cos(x-y)
 Sfrutto
           P(t) = E_0 T_0 \cdot \left[ \cos(wt + wt - \varphi) + \cos(wt - wt + \varphi) + \right] 
                                                     + \cos(\omega t - \frac{2}{3}\pi + \omega t - \frac{2}{3}\pi - \varphi) + \cos(\omega t - \frac{2}{3}\pi - \omega t + \frac{2}{3}\pi + \varphi) +
+ \cos(\omega t - \frac{4}{3}\pi + \omega t - \frac{4}{3}\pi - \varphi) + \cos(\omega t - \frac{4}{3}\pi - \omega t + \frac{4}{3}\pi + \varphi)
```

= Eo Io [ (ωs(2wt-φ)) + (cos(φ) +  $+ \cos(2\omega t - \frac{4}{3}\pi - \varphi) + \cos(\varphi) + \cos(2\omega t - \frac{8}{3}\pi - \varphi) + \cos(\varphi) = 3 \text{ En To } \cos(\varphi)$ 

T.S.D. = 0

da Pow di un sistema trifase e COSTANTE (auch se i gen somo N)

